
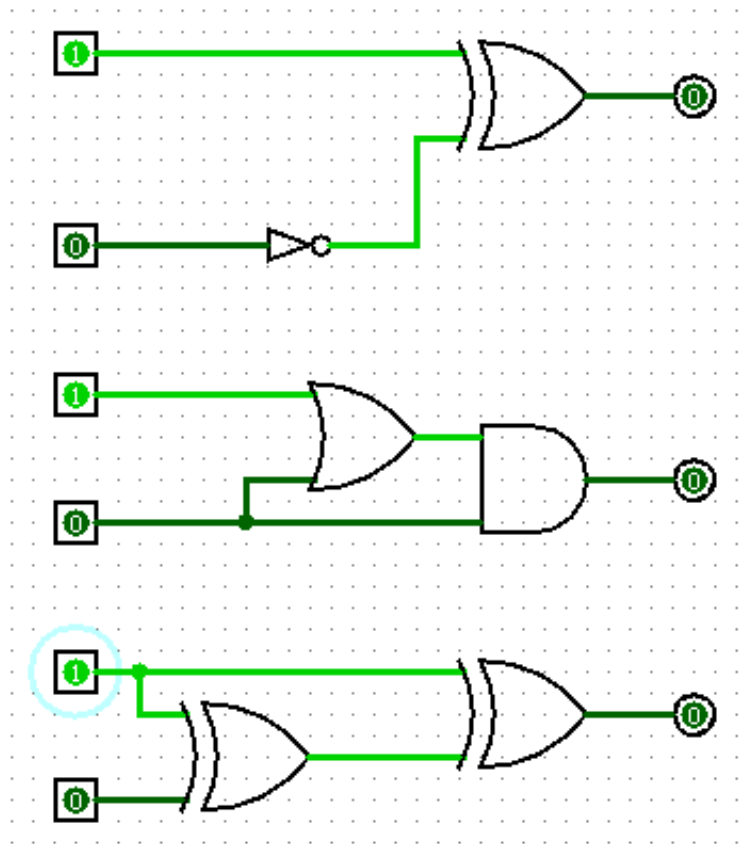


Xatamov Javohir U2210251

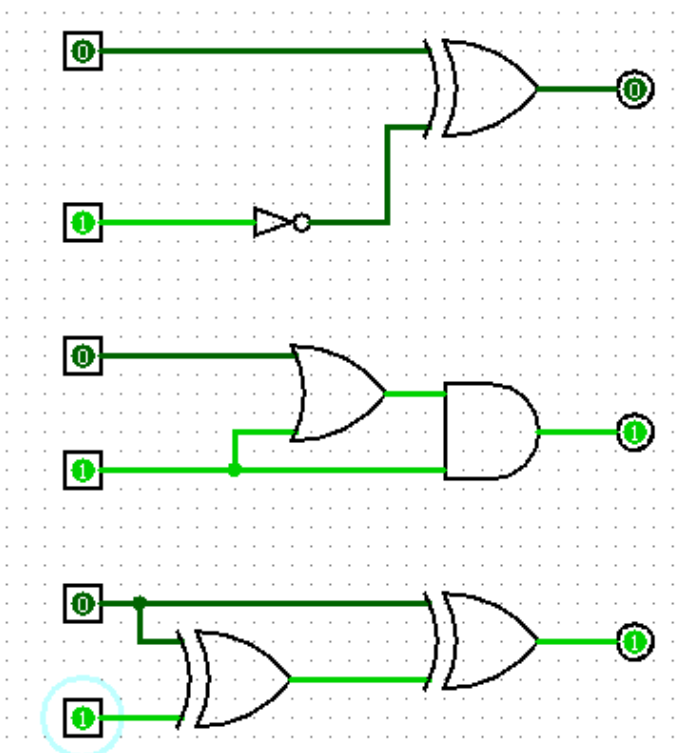
Circuits from figure 1. With 1 in upper input and 0 in lower input:



The same circuits but with 0 in upper input and 1 in lower input:



Circuit from figure 2:

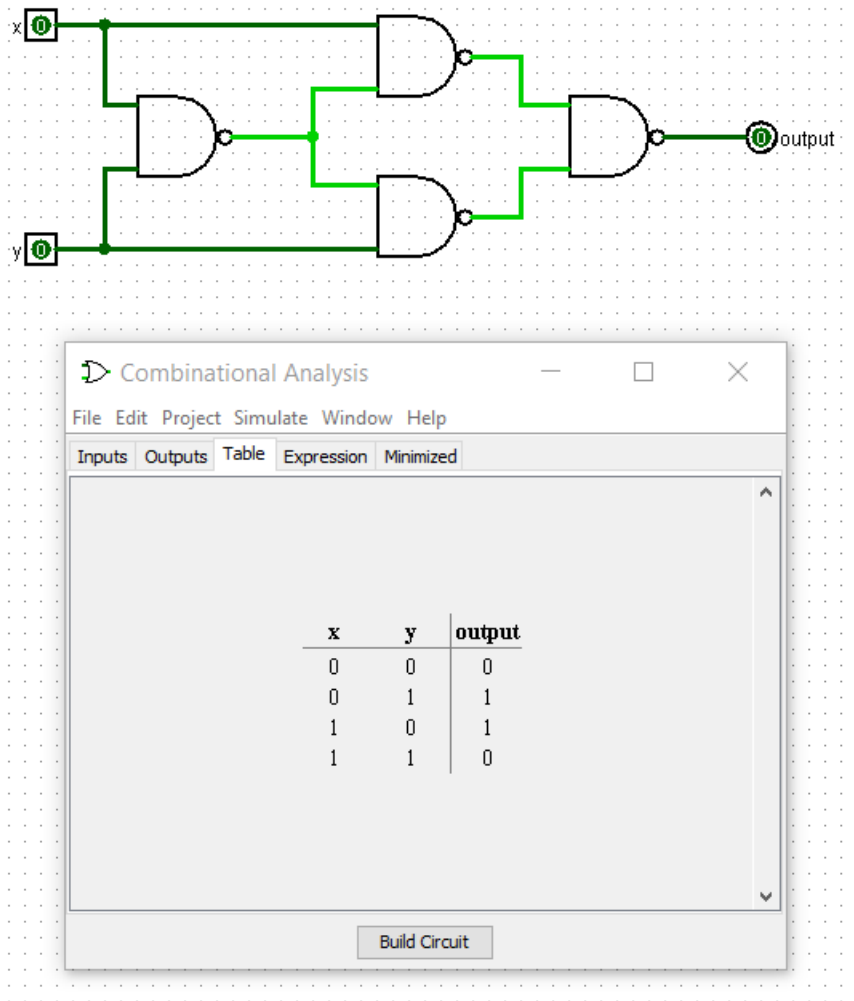

From its output values we can see that it represents XOR operator.