

Chap.14 Frequency Selective Circuits [Filters]

※ Chap. 12-13 Laplace Transform

$$X(s) = \int_0^{\infty} x(t) e^{-st} dt$$

where $s = \sigma + j\omega$ (complex number)


※ $s = j\omega$ in this part

- Frequency selective circuits are also called FILTERs.




§14.1 Some preliminaries

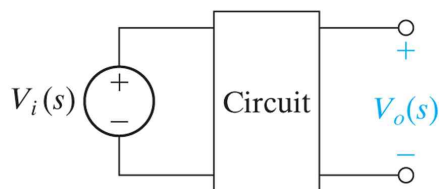- A circuit with voltage input and voltage output






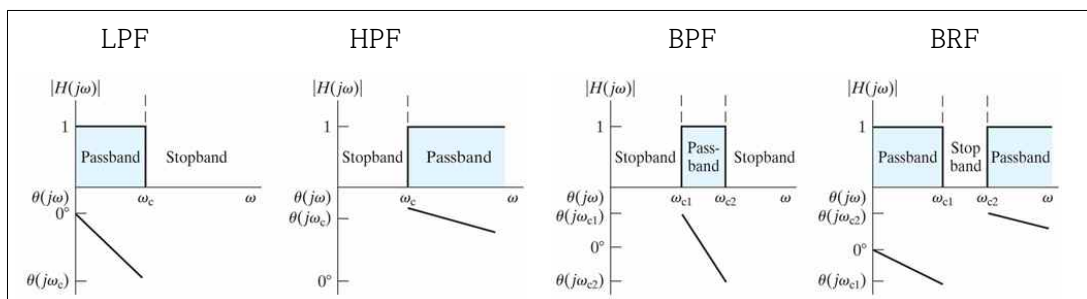- Frequency response
- passband, stopband, transition band
- cutoff frequency, low-pass filter, high-pass filter, bandpass filter, bandreject (or bandstop) filter
- Ideal Filters




- passive filter, active filter

§14.2 Low-Pass Filters (LPF)

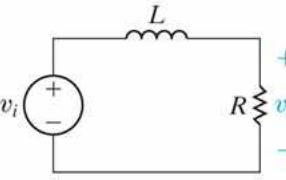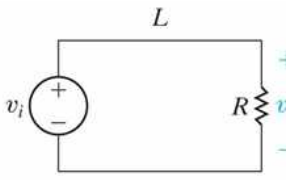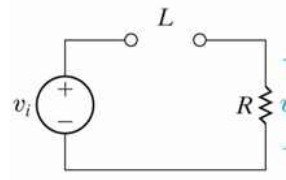a series RL LPF	equivalent circuit ($\omega = 0$)	equivalent circuit ($\omega = \infty$)
		

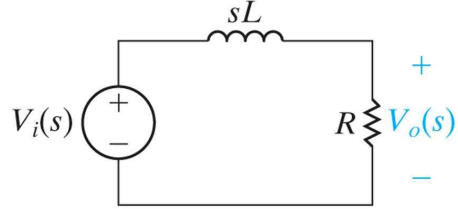- The series RL circuit – Quantitative Analysis



current $I(j\omega) = \frac{V_i(j\omega)}{j\omega L + R}$

output voltage $V_0(j\omega) = I(j\omega) \times R = \frac{V_i(j\omega)}{j\omega L + R} \times R$

the frequency response

$$H(j\omega) = \frac{V_0(j\omega)}{V_i(j\omega)} = \frac{R}{j\omega L + R} = \frac{R/L}{j\omega + R/L} \quad \text{Eq.(\#)}$$

the magnitude plot and the angle plot of the frequency response

$$|H(j\omega)| = \frac{R/L}{\sqrt{\omega^2 + (R/L)^2}}, \quad \theta(j\omega) = -\tan^{-1}\left(\frac{\omega L}{R}\right)$$

※ Defining the Cutoff Frequency (ω_c or f_c)

$$|H(j\omega_c)| = \frac{1}{\sqrt{2}} H_{\max}$$


the cutoff frequency of the series RL circuit

$$H_{\max} = |H(j0)| = 1$$


$$|H(j\omega_c)| = \frac{R/L}{\sqrt{\omega_c^2 + (R/L)^2}} = \frac{1}{\sqrt{2}} |1| \quad \therefore \omega_c = \frac{R}{L}$$

※ time constant : $\tau = \frac{L}{R}$

- Frequency response of an RL LPF

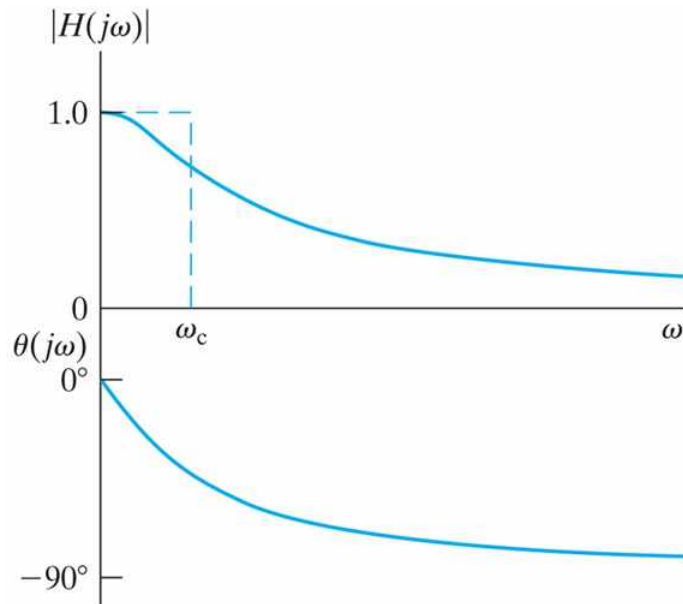

- A series RC circuit

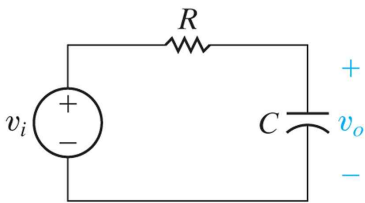

$$I(j\omega) = \frac{V_i(j\omega)}{R + \frac{1}{j\omega C}}$$

$$V_o(j\omega) = I(j\omega) \times \frac{1}{j\omega C} = \frac{V_i(j\omega)}{R + \frac{1}{j\omega C}} \times \frac{1}{j\omega C}$$



the frequency response

$$H(j\omega) = \frac{\frac{1}{j\omega C}}{R + \frac{1}{j\omega C}} = \frac{1}{j\omega RC + 1} = \frac{\frac{1}{RC}}{j\omega + \frac{1}{RC}} \quad \text{Eq. (##)}$$

(time constant : $\tau = RC$)




cutoff frequency : $\omega_c = \frac{1}{RC}$

※ Comparison [Low Pass Filters]

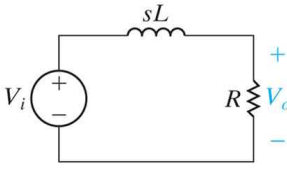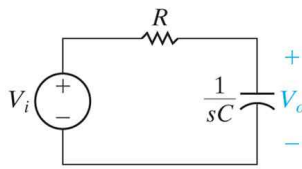
equation	Eq.(#)	Eq.##)
RL or RC	RL circuit	RC circuit
circuit		
Frequency Response	$H(j\omega) = \frac{R/L}{j\omega + R/L}$	$H(j\omega) = \frac{\frac{1}{RC}}{j\omega + \frac{1}{RC}}$
Time Constant	$\tau = \frac{L}{R} \quad [\text{sec}]$	$\tau = RC \quad [\text{sec}]$
Cutoff Frequency	$\omega_c = \frac{R}{L} \quad [\text{rad/sec}]$ (or $f_c = \frac{1}{2\pi} \left(\frac{R}{L} \right) \quad [\text{Hz}]$)	$\omega_c = \frac{1}{RC} \quad [\text{rad/sec}]$ (or $f_c = \frac{1}{2\pi} \left(\frac{1}{RC} \right) \quad [\text{Hz}]$)
Remark	$H(j\omega) = \frac{\text{constant}}{j\omega + \text{constant}} = \frac{\omega_c}{j\omega + \omega_c}$ 1. General form of first-order LPF 2. one memory circuits 3. first-order differential equation in time domain 4. frequency response in frequency domain	

§14.3 High-Pass Filters (HPF)


- A series RC circuit

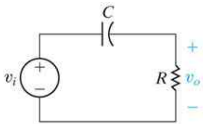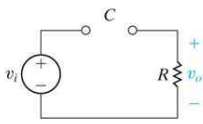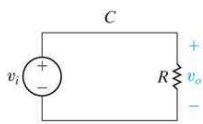a series RC HPF	equivalent circuit ($\omega = 0$)	equivalent circuit ($\omega = \infty$)
		

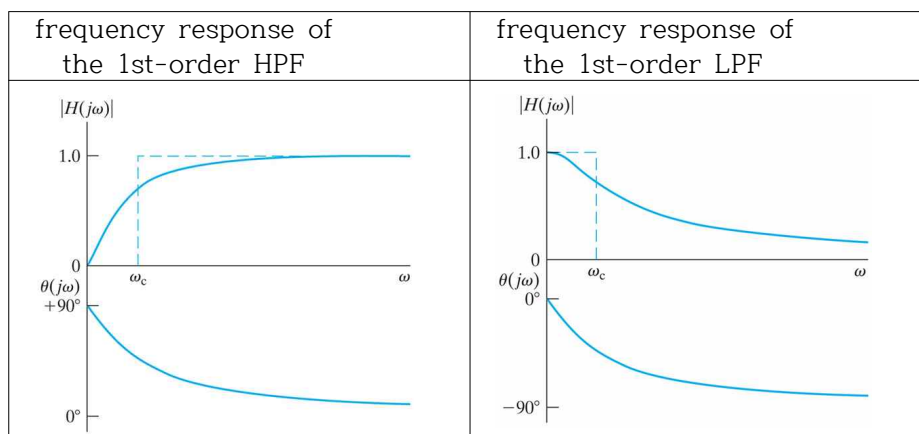- Frequency response of the first-order RC HPF



- the first-order RC HPF

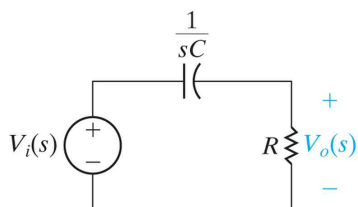

$$I(j\omega) = \frac{V_i(j\omega)}{\frac{1}{j\omega C} + R}$$

$$V_o(j\omega) = I(j\omega) \times R = \frac{V_i(j\omega)}{\frac{1}{j\omega C} + R} \times R = \frac{R}{\frac{1}{j\omega C} + R} \times V_i(j\omega)$$

$$= \frac{j\omega RC}{1 + j\omega RC} \times V_i(j\omega) = \frac{j\omega}{j\omega + \frac{1}{RC}} \times V_i(j\omega)$$

- the frequency response

$$H(j\omega) = \frac{V_o(j\omega)}{V_i(j\omega)} = \frac{j\omega}{j\omega + 1/RC} \quad \text{Eq. (*)}$$


the magnitude and the angle of the frequency response

$$|H(j\omega)| = \frac{\omega}{\sqrt{\omega^2 + (1/RC)^2}} \quad , \quad \theta(j\omega) = 90^\circ - \tan^{-1} \omega RC$$

the cutoff frequency : $\omega_c = \frac{1}{RC}$ (* time constant : $\tau = RC$)

※ Same cutoff frequency (or time constant) with LPF



- (example) A series RL HPF

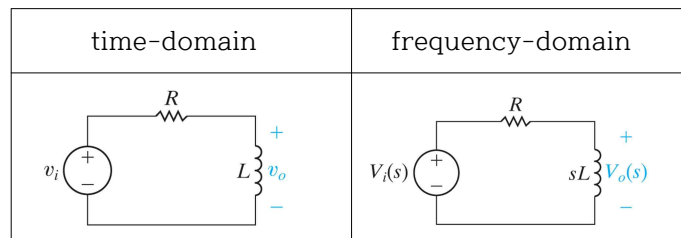




frequency response : $H(j\omega) = \frac{j\omega}{j\omega + R/L}$ Eq. (**)

cutoff frequency : $\omega_c = \frac{R}{L}$


※ Comparison [High Pass Filters]

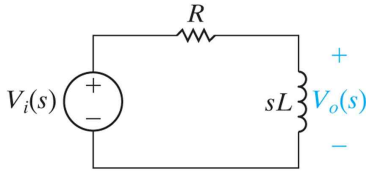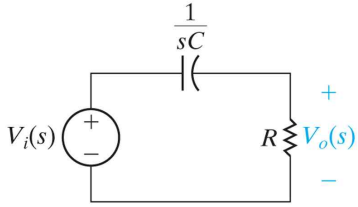equation	Eq.(**)	Eq.(*)
RL or RC	RL circuit	RC circuit
circuit		
Frequency Response	$H(j\omega) = \frac{j\omega}{j\omega + R/L}$	$H(j\omega) = \frac{j\omega}{j\omega + 1/RC}$
Time Constant	$\tau = \frac{L}{R} \quad [\text{sec}]$	$\tau = RC \quad [\text{sec}]$
Cutoff Frequency	$\omega_c = \frac{R}{L} \quad [\text{rad/sec}]$ (or $f_c = \frac{1}{2\pi} \left(\frac{R}{L} \right) \quad [\text{Hz}]$)	$\omega_c = \frac{1}{RC} \quad [\text{rad/sec}]$ (or $f_c = \frac{1}{2\pi} \left(\frac{1}{RC} \right) \quad [\text{Hz}]$)
Remark	$H(j\omega) = \frac{j\omega}{j\omega + \text{constant}} = \frac{j\omega}{j\omega + \omega_c}$ 1. General form of first-order HPF 2. one memory circuits 3. first-order differential equation in time domain 4. frequency response in frequency domain	


(Example) LPF (R-C Low Pass Filter)

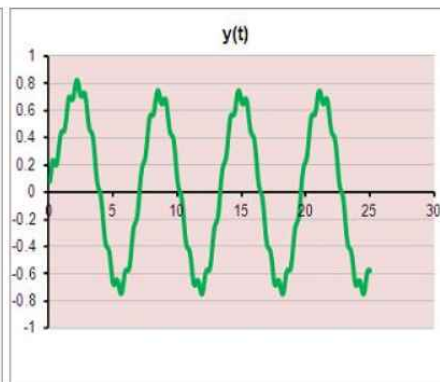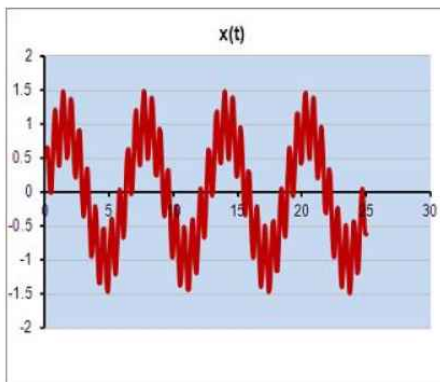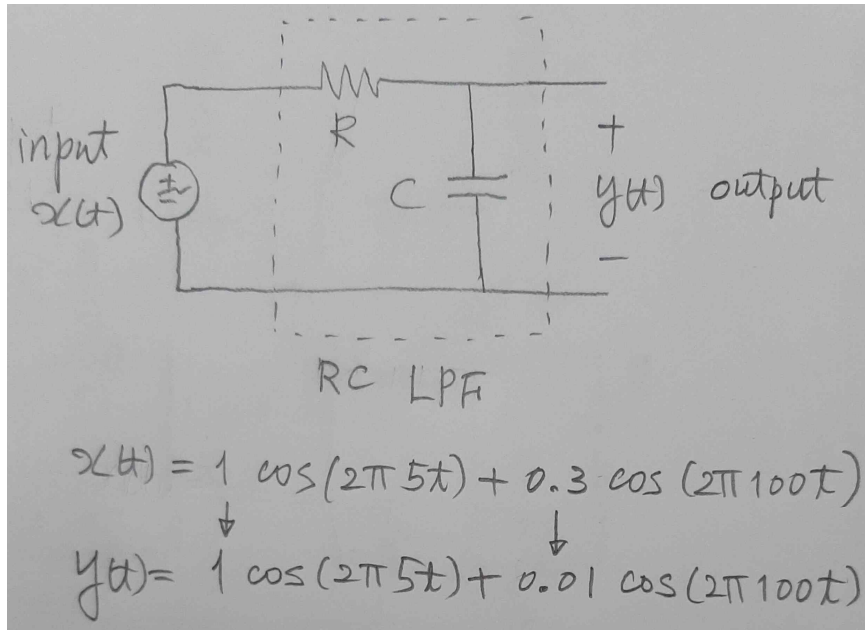

(Example) LPF, HPF

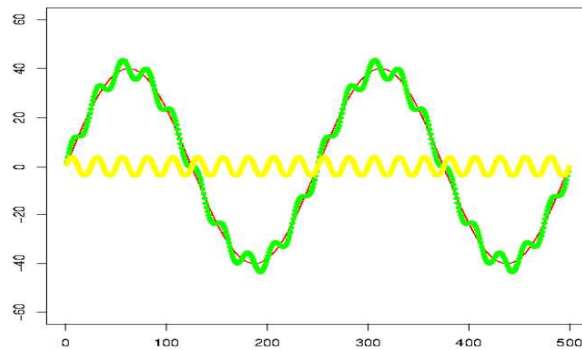

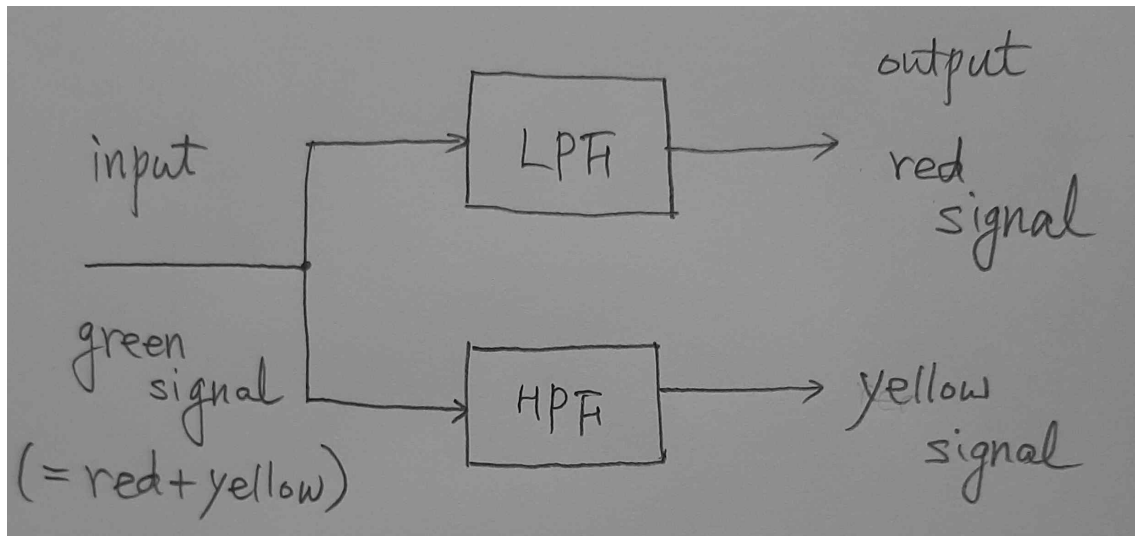
green signal = red signal (low frequency signal)
+ yellow signal (high frequency signal)




(Example of LPF) ECG (ElectroCardioGraph)

period $T = 0.75$ sec / heart rate = 80/minute


(a) measured signal

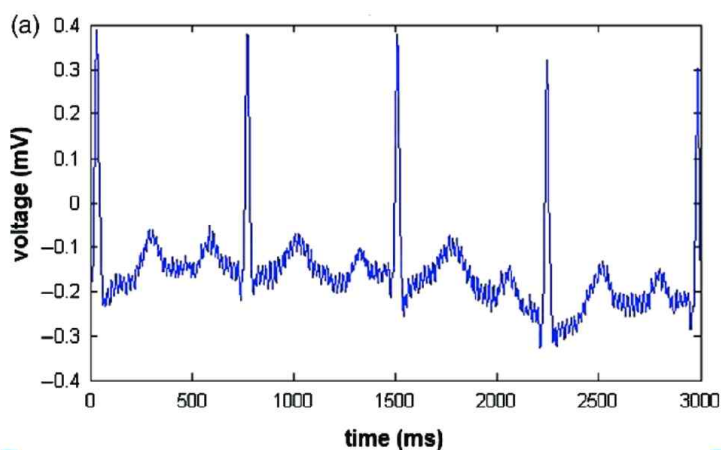

(b) filtered signal

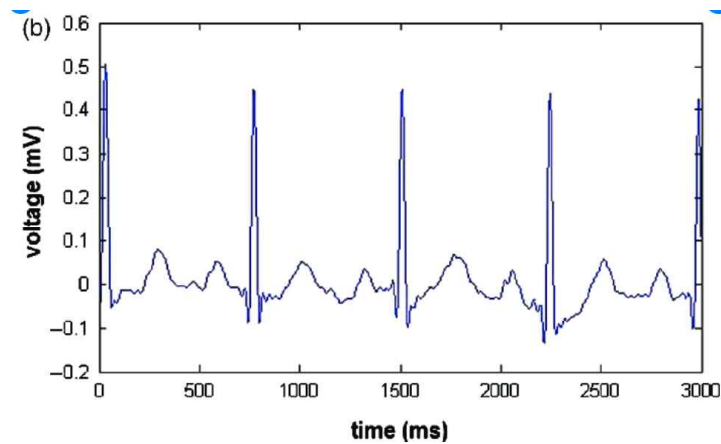

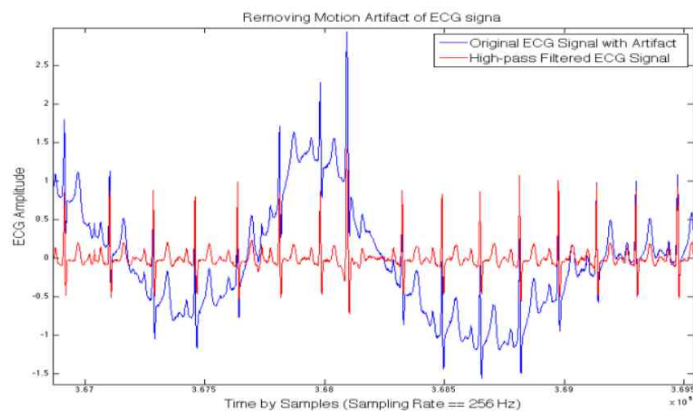(Example of HPF) ECG (ElectroCardioGraph)




§14.4 Bandpass Filters (BPF)


- A series RLC bandpass filter

a series RLC BPF	equivalent circuit ($\omega = 0$)	equivalent circuit ($\omega = \infty$)

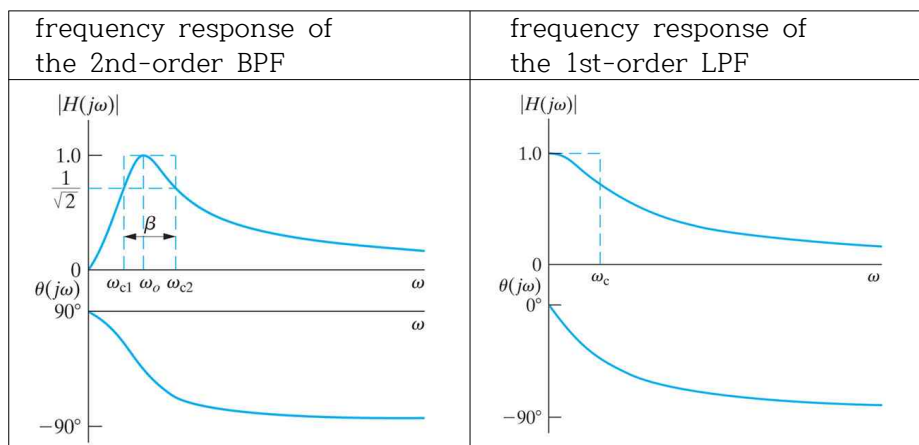- Frequency response of the second-order RLC BPF



The series RLC Circuit

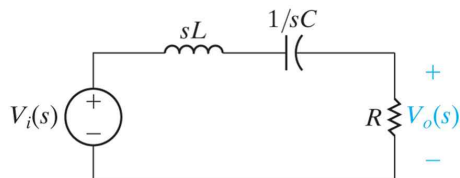

- frequency response

$$\begin{aligned}
 H(j\omega) &= \frac{V_o(j\omega)}{V_i(j\omega)} = \frac{R}{R + j\omega L + \frac{1}{j\omega C}} = \frac{R}{R + j(\omega L - \frac{1}{\omega C})} \\
 &= \frac{(R/L)(j\omega)}{(j\omega)^2 + (R/L)(j\omega) + (1/LC)}
 \end{aligned}$$

$$\text{(magnitude)} \quad |H(j\omega)| = \frac{\omega(R/L)}{\sqrt{[(1/LC) - \omega^2]^2 + [\omega(R/L)]^2}}$$

$$\text{(phase)} \quad \theta(j\omega) = 90^\circ - \tan^{-1} \left[\frac{\omega(R/L)}{(1/LC) - \omega^2} \right]$$

- center frequency : ω_0 [the frequency of max $|H(j\omega)|$]

When $(1/LC) - \omega^2 = 0$, $|H(j\omega)|$ is maximum.

$$\omega_0 = \sqrt{\frac{1}{LC}} \quad (\text{i.e., } f_0 = \frac{1}{2\pi\sqrt{LC}} \text{ in physics class})$$

(At the center frequency, $j\omega_0 L + \frac{1}{j\omega_0 C} = 0$.)

That is, at $\omega = \omega_0$, $Z = R + j\omega_0 L + \frac{1}{j\omega_0 C} = R$.

So, when $\omega = \omega_0$, the RLC circuit will a resistor circuit.)

※ Resonant circuit in physics class

- cutoff frequencies : ω_{c1} and ω_{c2}

$$H_{\max} = |H(j\omega_0)| = 1$$

frequencies ω_{c1} and ω_{c2} for $|H(j\omega_{c1})| = |H(j\omega_{c2})| = \frac{1}{\sqrt{2}} H_{\max}$

$$\omega_{c1} = -\frac{R}{2L} + \sqrt{\left(\frac{R}{2L}\right)^2 + \left(\frac{1}{LC}\right)}$$

$$\omega_{c2} = \frac{R}{2L} + \sqrt{\left(\frac{R}{2L}\right)^2 + \left(\frac{1}{LC}\right)}$$

- center frequency and cutoff frequencies

$$\omega_0 = \sqrt{\omega_{c1} \cdot \omega_{c2}} = \sqrt{\frac{1}{LC}}$$



- bandwidth : β

$$\beta = \omega_{c2} - \omega_{c1} = \frac{R}{L}$$

- Quality Factor : Q

$$Q = \frac{\omega_0}{\beta} = \sqrt{\frac{L}{CR^2}}$$



- a parallel RLC BPF

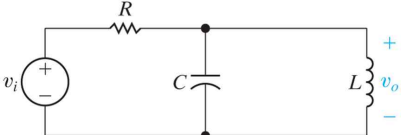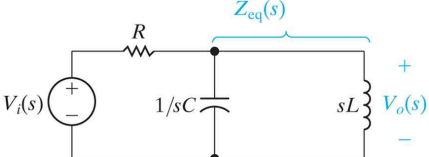a parallel RLC BPF	the frequency-domain equivalent
	

- frequency response

$$H(j\omega) = \frac{\frac{j\omega}{RC}}{j\omega^2 + \frac{j\omega}{RC} + \frac{1}{LC}}$$

- Bandpass Filters

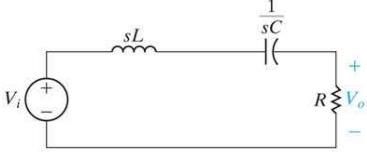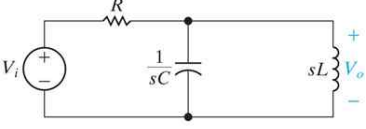a series RLC BPF	a parallel RLC BPF
 $H(s) = \frac{(R/L)s}{s^2 + (R/L)s + 1/LC}$ $\omega_o = \sqrt{1/LC} \quad \beta = R/L$	 $H(s) = \frac{s/RC}{s^2 + s/RC + 1/LC}$ $\omega_o = \sqrt{1/LC} \quad \beta = 1/RC$

- General form of the frequency response for BPF


$$H(j\omega) = \frac{\text{constant} \times (j\omega)}{(j\omega)^2 + \text{constant} \times (j\omega) + \text{constant}}$$

$$= \frac{\beta(j\omega)}{(j\omega)^2 + \beta(j\omega) + \omega_0^2}$$

$$\text{where } \omega_0 = \sqrt{\frac{1}{LC}}$$


$$\text{and } \beta = \frac{R}{L} \quad (\text{series circuit}) \quad \text{or} \quad \beta = \frac{1}{RC} \quad (\text{parallel circuit})$$

(Example of BPF) Channel selector of TV

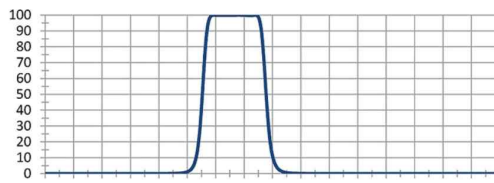

(Example of BPF)

choose blue color light from white light

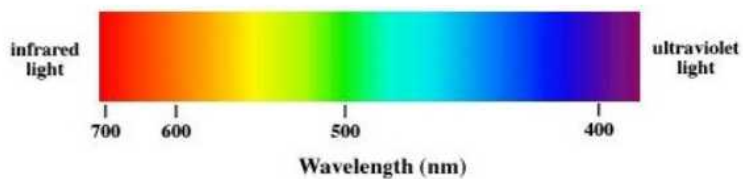


Type of Radiation Frequency Range (Hz) Wavelength Range

gamma-rays	$10^{20} - 10^{24}$	$< 10^{-12}$ m
x-rays	$10^{17} - 10^{20}$	1 nm - 1 pm
ultraviolet	$10^{15} - 10^{17}$	400 nm - 1 nm
visible	$4 - 7.5 \times 10^{14}$	750 nm - 400 nm
near-infrared	$1 \times 10^{14} - 4 \times 10^{14}$	2.5 μ m - 750 nm
infrared	$10^{13} - 10^{14}$	25 μ m - 2.5 μ m
microwaves	$3 \times 10^{11} - 10^{13}$	1 mm - 25 μ m
radio waves	$< 3 \times 10^{11}$	> 1 mm




red color : lower frequency (4×10^{14} Hz = 400 THz)

violet color : higher frequency (7.5×10^{14} Hz = 750 THz)

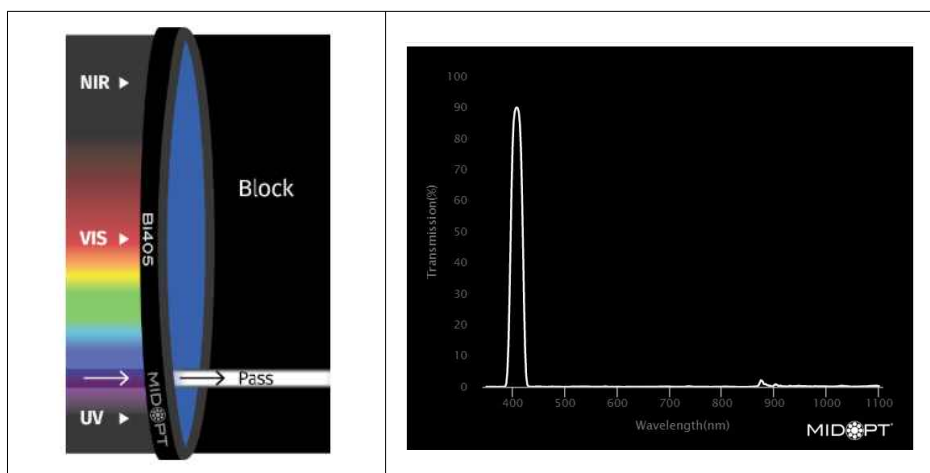
How can we select violet light from the sun light? (Bandpass) Filter




§14.5 Bandreject Filter [BRF] (or Bandstop Filter [BSF])

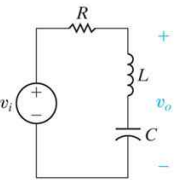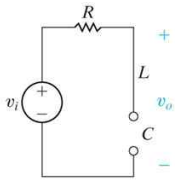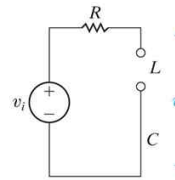a series RLC BRF	equivalent circuit ($\omega = 0$)	equivalent circuit ($\omega = \infty$)
		

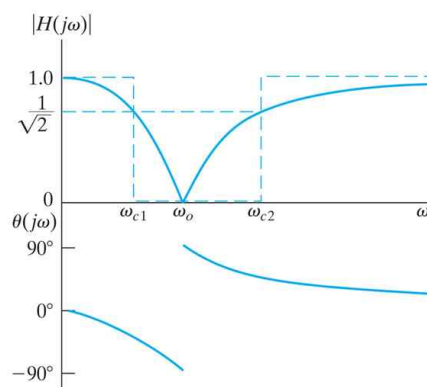- Frequency Response of the series RLC BRF



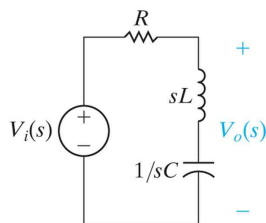- frequency-domain equivalent of the series RLC BRF



- frequency response of the series RLC BRF

$$H(j\omega) = \frac{(j\omega)^2 + \frac{1}{LC}}{(j\omega)^2 + (R/L)(j\omega) + (1/LC)}$$


- Summary

LPF	$H(j\omega) = \frac{\text{constant}}{(j\omega) + \text{constant}} \quad (\#)$
HPF	$H(j\omega) = \frac{(j\omega)}{(j\omega) + \text{constant}}$
BPF	$H(j\omega) = \frac{\text{constant} \times (j\omega)}{(j\omega)^2 + \text{constant} \times (j\omega) + \text{constant}}$
BRF	$H(j\omega) = \frac{(j\omega)^2 + \text{constant}}{(j\omega)^2 + \text{constant} \times (j\omega) + \text{constant}}$

Chap.15 Active Filter Circuits

※ active : use active elements (op amp)

§15.1 First-Order Active Low-Pass Filter

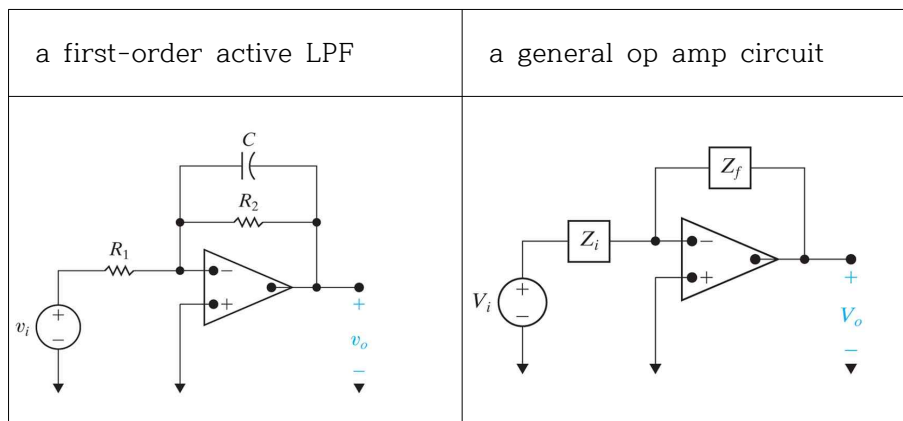

- Frequency Response

$$\begin{aligned}
 H(j\omega) &= -\frac{Z_f}{Z_i} = -\frac{R_2 \parallel \left(\frac{1}{j\omega C}\right)}{R_1} \\
 &= -\frac{R_2}{R_1} \frac{\frac{1}{R_2 C}}{j\omega + \frac{1}{R_2 C}} \equiv -K \frac{\omega_c}{j\omega + \omega_c} \quad (##)
 \end{aligned}$$

K : gain, ω_c : cutoff frequency

※ same type with Eq.(#) or Eq.##), that is, Low Pass Filter

※ If this frequency response, $\frac{\text{constant}}{j\omega + \text{constant}}$, is given,
we can have several methods to install in hardware.

- A note about Frequency Response Plots

the transfer function magnitude versus frequency

the transfer function phase angle versus frequency

- Bode plots

1. Instead of using a linear axis for the frequency value,
a Bode plot uses a logarithmic axis.
2. Instead of plotting the absolute magnitude of the transfer function
versus frequency, the Bode magnitude is plotted in decibels(dB)
versus the log of the frequency.

- dB (decibel)

$$A_{dB} = 20 \log_{10} |H(j\omega)| \quad (\text{magnitude ratio})$$


$$\ast \text{ power ratio : } P_{dB} = 10 \log_{10} \frac{P}{P_{ref}}$$

$$\text{amplitude ratio : } A_{dB} = 20 \log_{10} \frac{A}{A_{ref}} \quad (\text{Generally we use this.})$$

$$\ast 20 \log_{10} \left| \frac{1}{\sqrt{2}} \right| = -3 \text{ dB} \quad (\text{important})$$

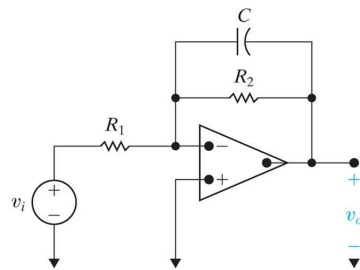(example)

Design an active LPF using the circuit ($R_1=1\Omega$).



the cutoff frequency : 1 rad/sec

the gain in the passband : 1


(solution)

$$R_2 = 1\Omega, C = 1F$$


the frequency response

$$H(j\omega) = -\frac{1}{j\omega + 1}$$

the Bode magnitude plot (prototype)

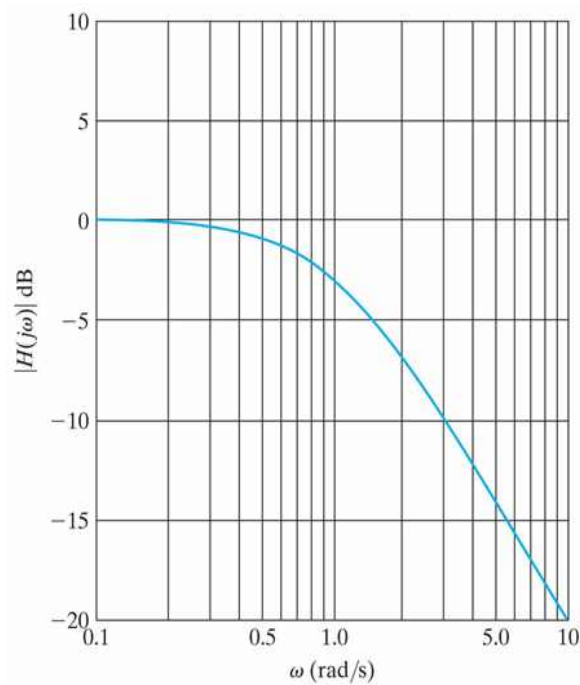

● First-Order Active High-Pass Filter

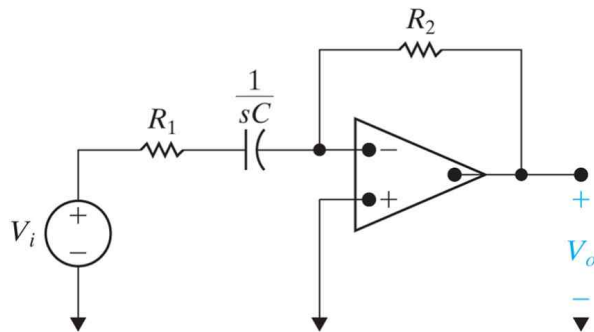

- Frequency Response


$$H(j\omega) = - \frac{R_2}{R_1 + \frac{1}{j\omega C}} = -K \frac{j\omega}{j\omega + \omega_c}$$

where

$$\text{Gain } K = \frac{R_2}{R_1}$$

$$\text{and Cutoff frequency } \omega_c = \frac{1}{R_1 C}$$

(Example) Design an Active HPF

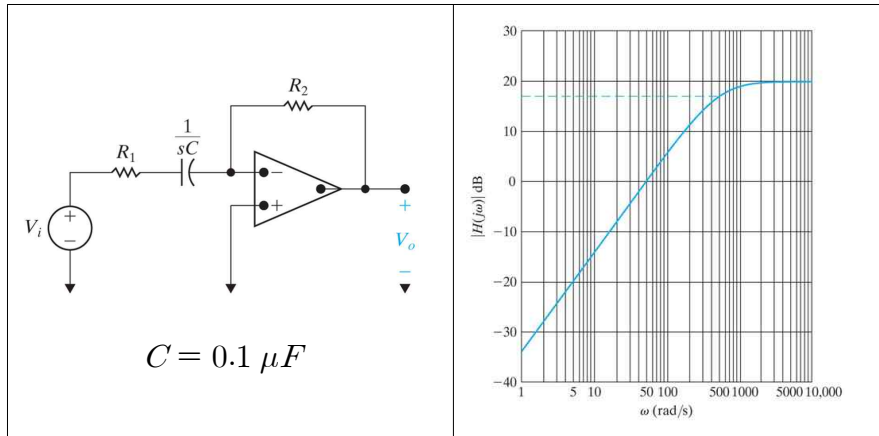

(1) cutoff frequency (-3dB frequency) :

from the graph $\omega_c = 500 \text{ rad/sec}$

$$\omega_c = \frac{1}{R_1 C},$$

$$\text{so } R_1 = \frac{1}{\omega_c C} = \frac{1}{500 \times (0.1 \times 10^{-6})} = 20,000 = 20 \text{ k}\Omega$$

(2) gain in the passband : $A_{dB} = 20 \text{ dB}$

$$A_{dB} = 20 \log_{10} \frac{V_0}{V_i} = 20 \log_{10} K$$


$$\therefore K = 10^{\frac{A_{dB}}{20}} = 10^{\frac{20}{20}} = 10^1 = 10$$

$$K = \frac{R_2}{R_1} \quad \therefore \text{Since } R_1 = 20 \text{ k}\Omega, \quad R_2 = 200 \text{ k}\Omega$$

Therefore,


$$C = 0.1 \mu F, R_1 = 20 \text{ k}\Omega, \text{ and } R_2 = 200 \text{ k}\Omega$$

The circuit of the active HPF

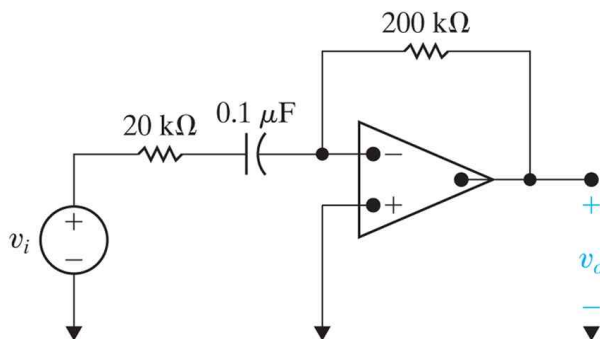


§15.3 Op Amp Bandpass and Bandreject Filters

- Bandpass Filter

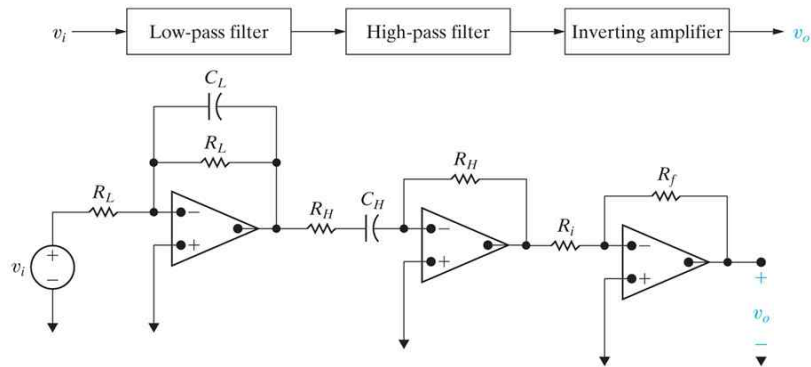

- the Bode magnitude plot

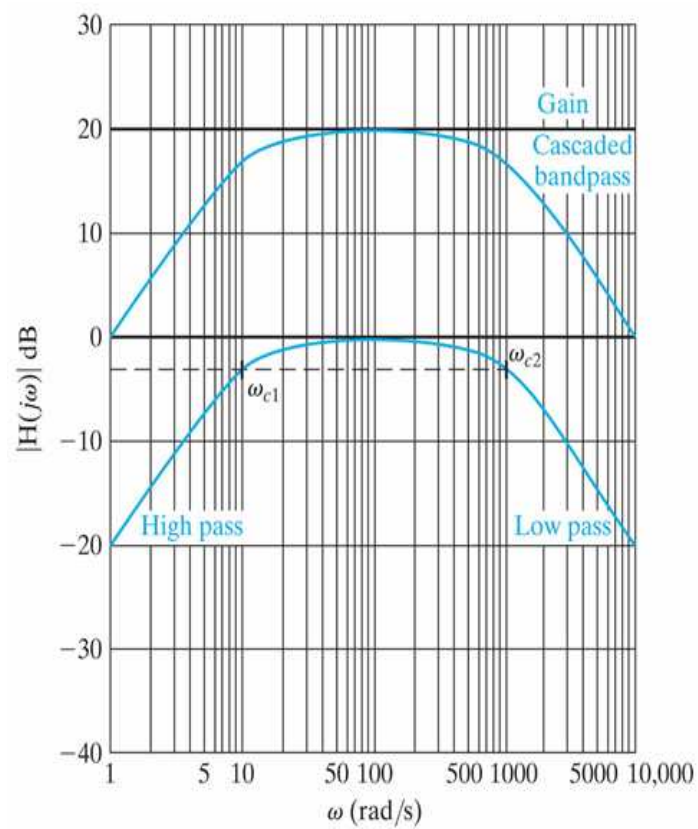



※ broadband

§15.4 Higher Order Op Amp Filters

- Cascading Identical Filters

$$H(j\omega) = \left(\frac{-1}{j\omega + 1} \right) \left(\frac{-1}{j\omega + 1} \right) \cdots \left(\frac{-1}{j\omega + 1} \right)$$



$$= \frac{(-1)^n}{(j\omega + 1)^n}$$

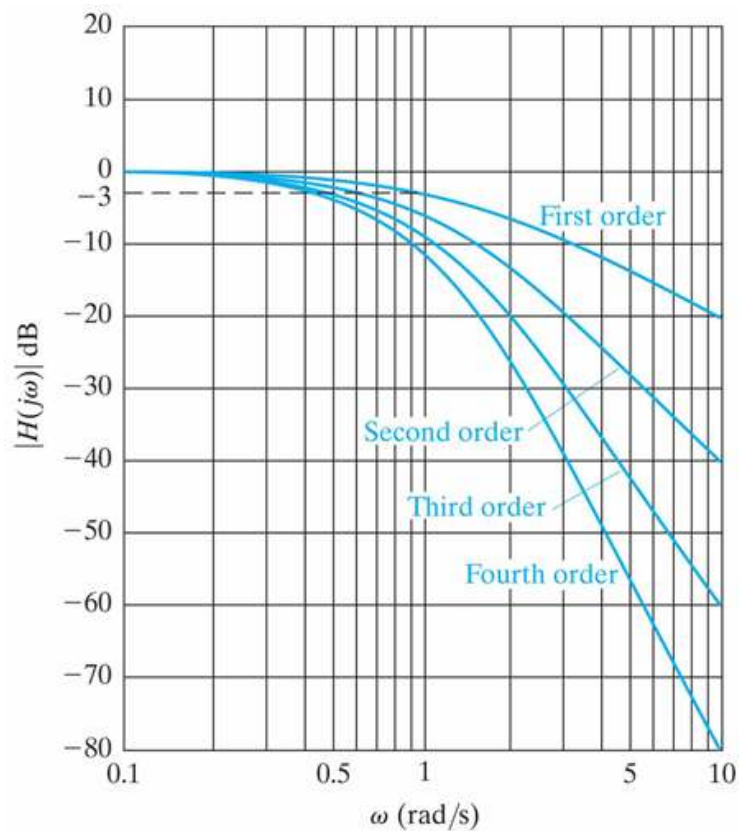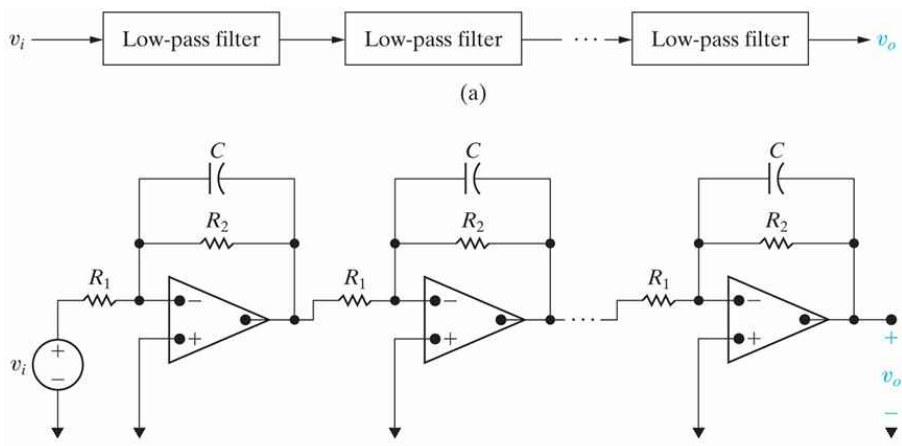


● Butterworth Filter

The magnitude of the transfer function of a unity-gain Butterworth LPF

$$|H(j\omega)| = \frac{1}{\sqrt{1 + \left(\frac{\omega}{\omega_c}\right)^{2n}}}$$

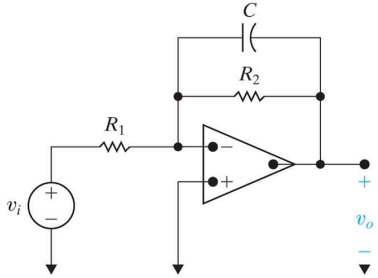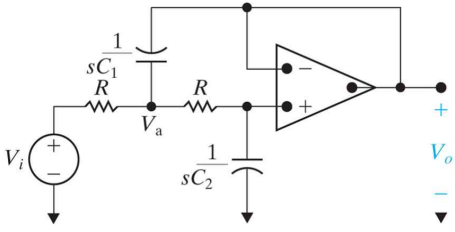first-order LPF	second-order LPF
	
$H(j\omega) = -\frac{R_2}{R_1} \frac{\frac{1}{R_2 C}}{j\omega + \frac{1}{R_2 C}}$	$H(j\omega) = \frac{\frac{1}{R^2 C_1 C_2}}{(j\omega)^2 + \frac{2}{R C_1} (j\omega) + \frac{1}{R^2 C_1 C_2}}$

(example) a 4th-order Butterworth LPF

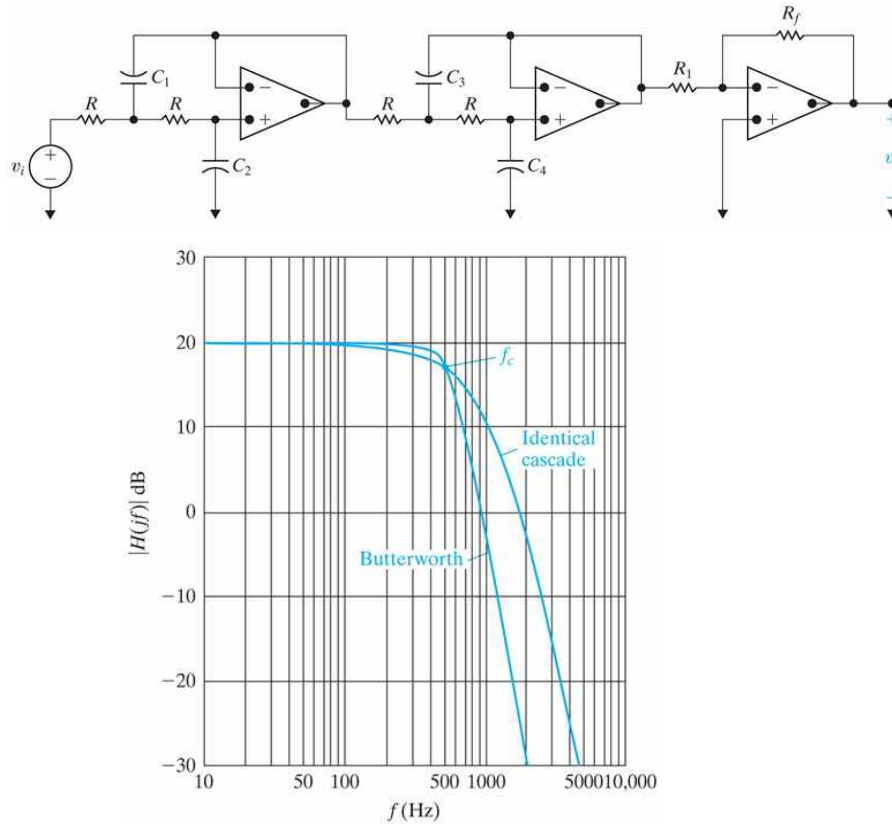

- Butterworth HPF

first-order HPF	second-order HPF
$H(j\omega) = -\frac{R_2}{R_1} \frac{(j\omega)}{(j\omega) + \frac{1}{R_1 C}}$	$H(j\omega) = \frac{(j\omega)^2}{(j\omega)^2 + \frac{2}{R_2 C} (j\omega) + \frac{1}{R_1 R_2 C^2}}$

※ We can connect first- and second-order LPFs and/or HPFs in cascade to make a higher order Butterworth filters.